



GEBZE TECHNICAL UNIVERSITY

ELEC 335


LAB 3 REPORT

BERKAY TÜRK


171024024

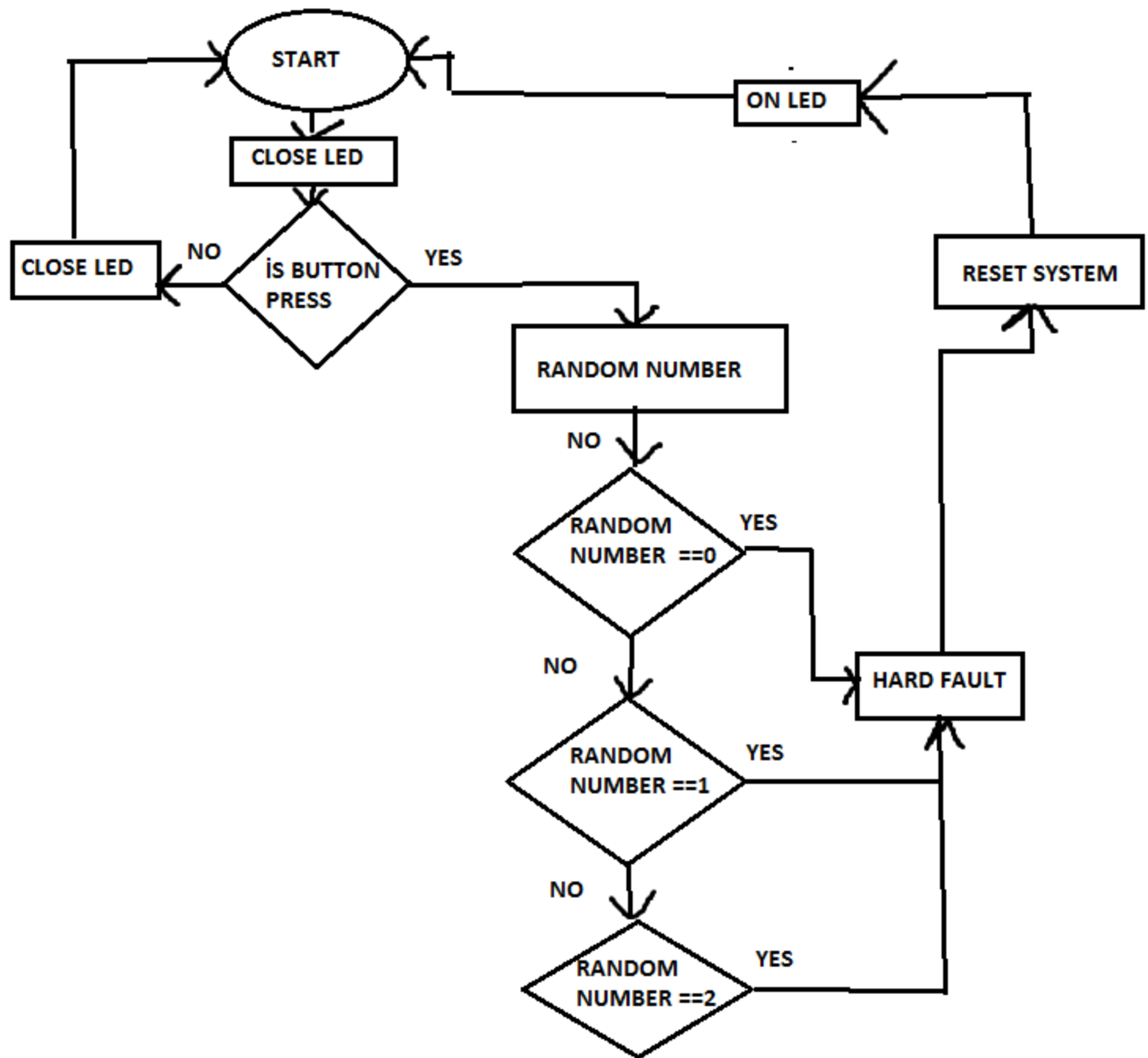PROBLEM 1:

Create the Hard Fault Handler and some faults.



Flowchart

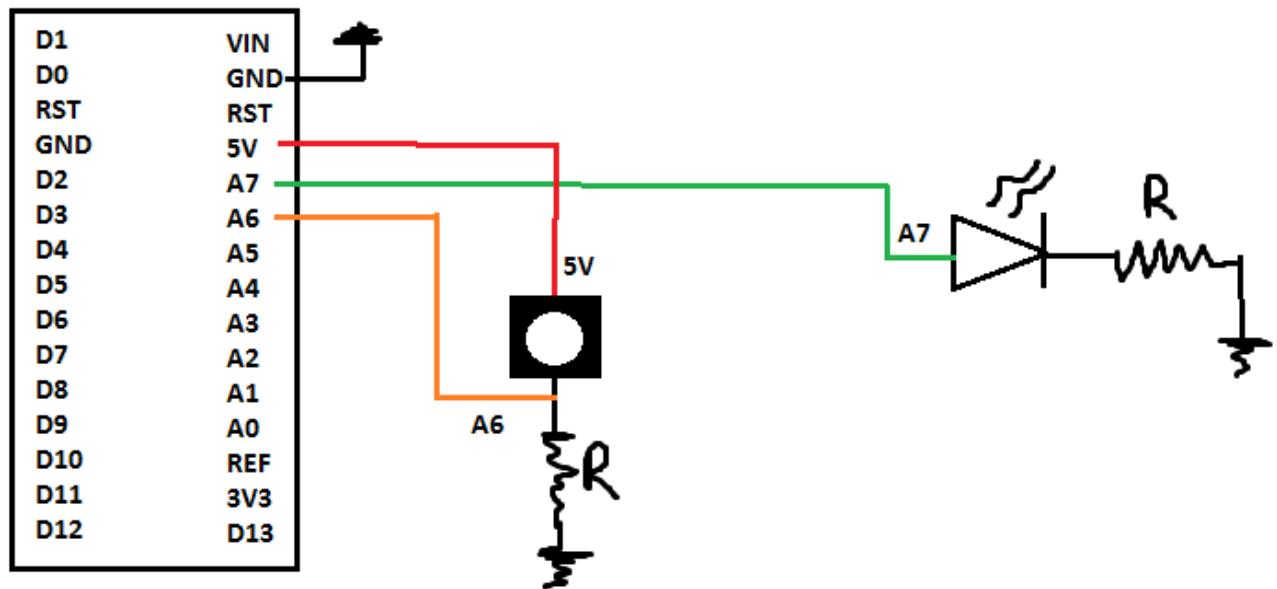


Connection Diagram

1.Problem video:


<https://youtu.be/n6Et8FL-XDw>

PROBLEM 2:

interrupt and hard fault creating.

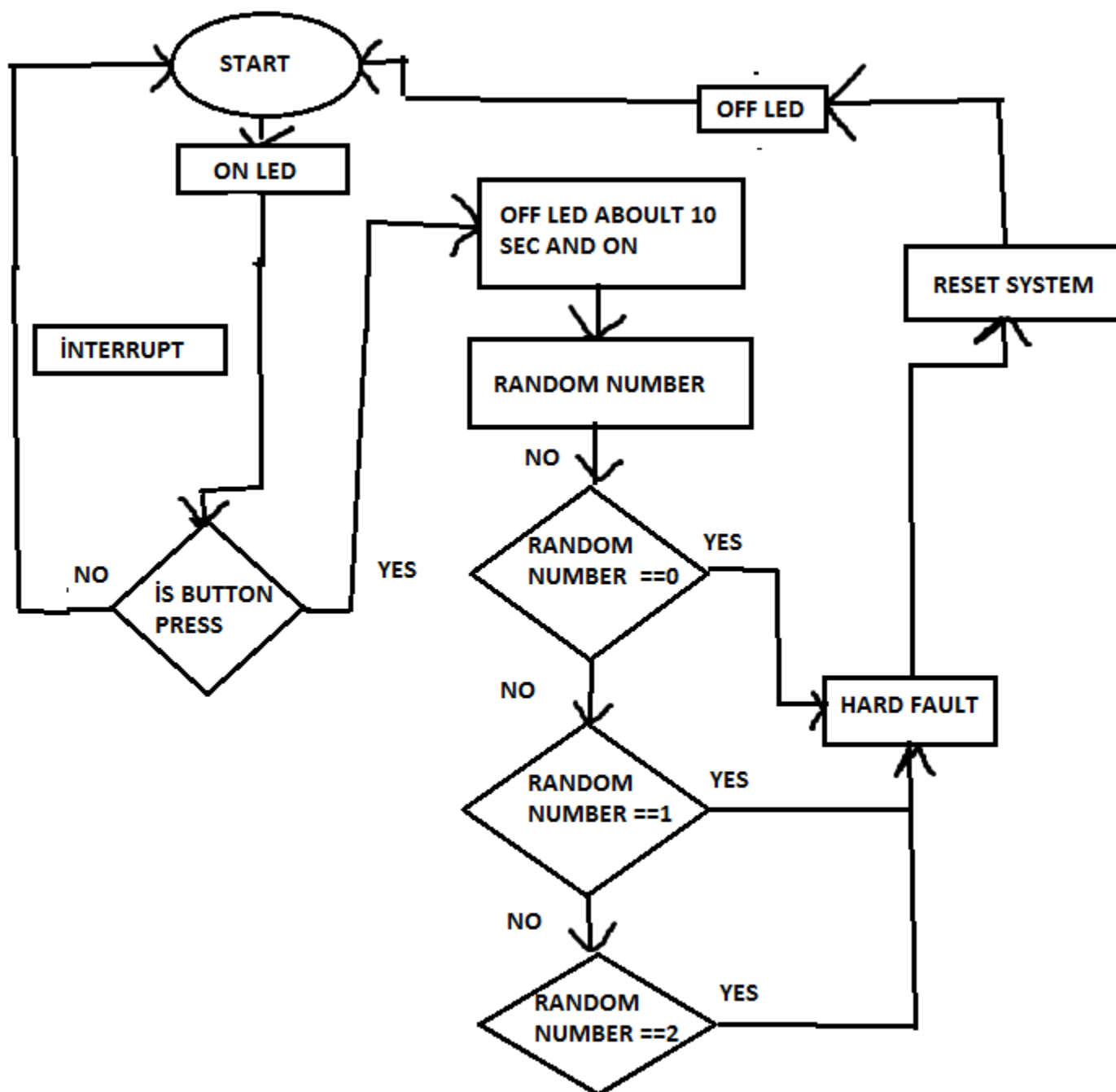

Flowchart

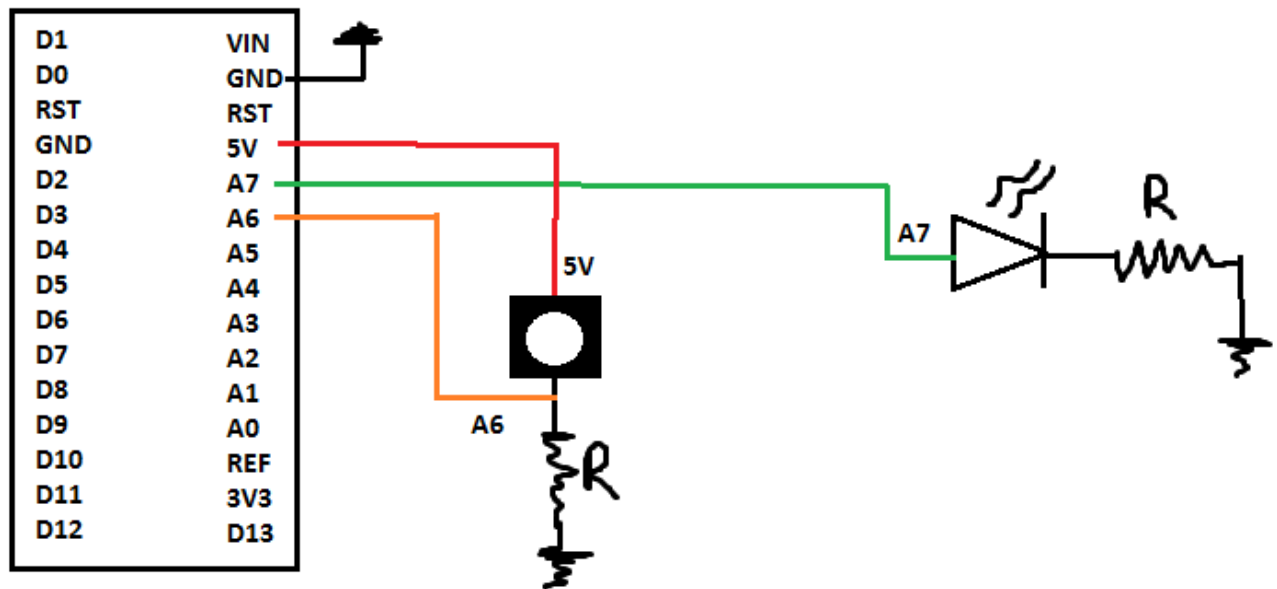


Connection Diagram

2.Problem video:


<https://youtu.be/RsXsTNfSUXo>

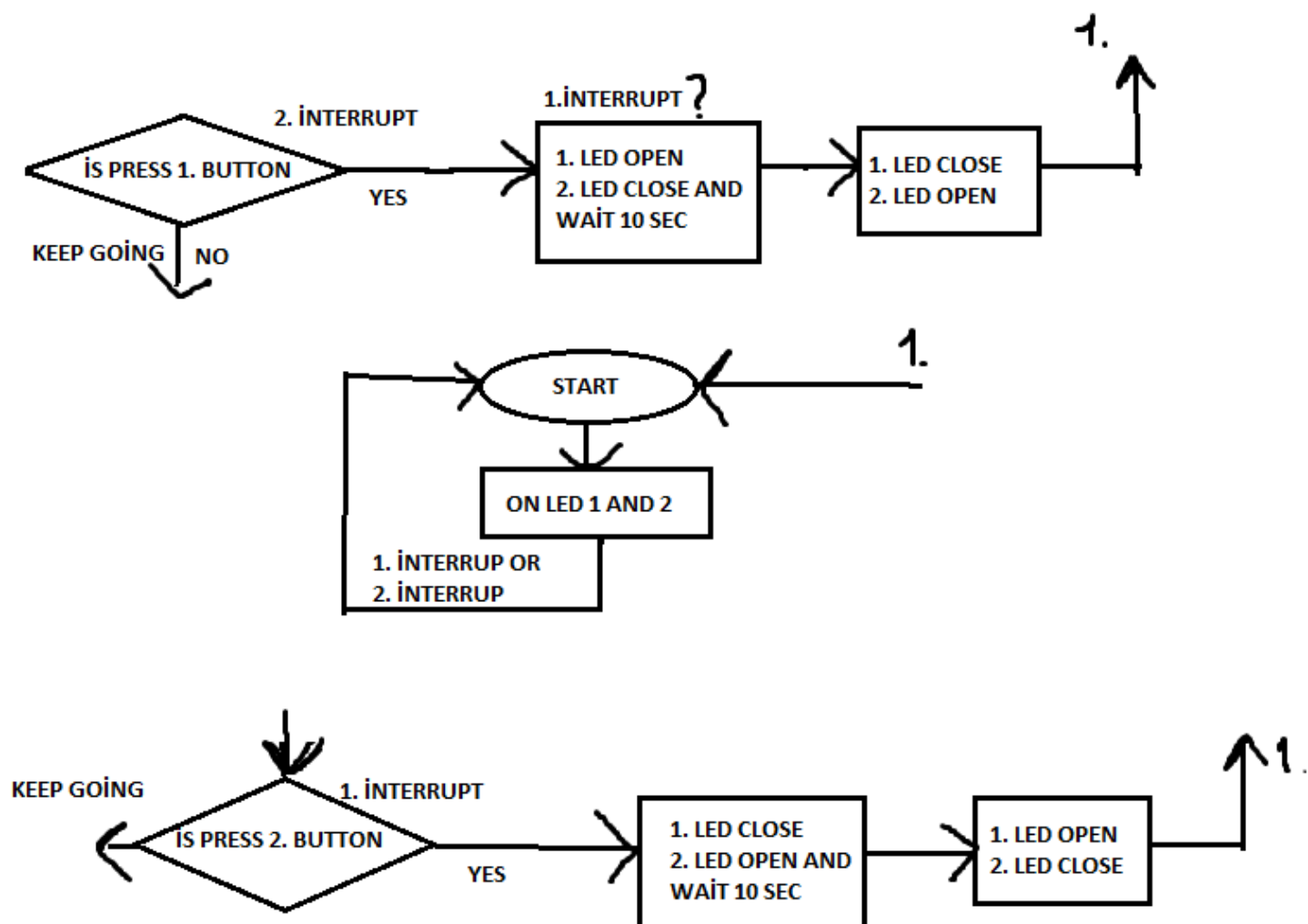PROBLEM 3:

Connect two leds and two buttons and first turn on/off high priority interrupt.



Flowchart

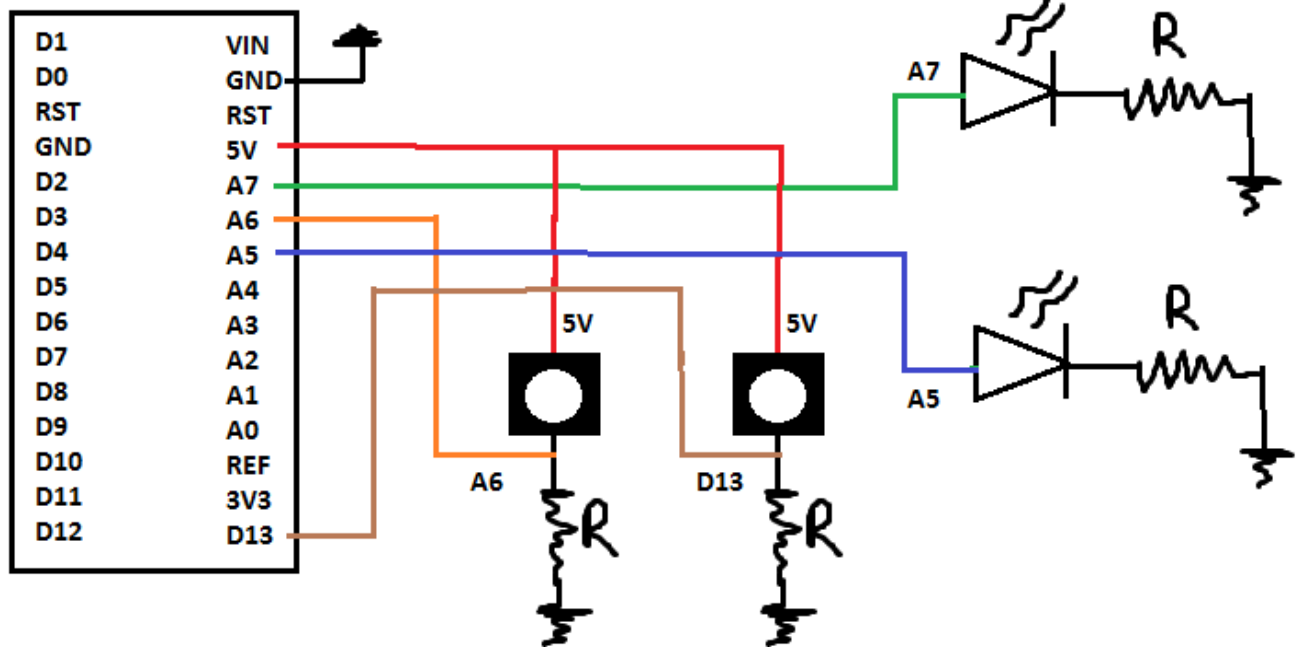

Connection Diagram

3.Problem video:

<https://youtu.be/jY2qsupsOTk>